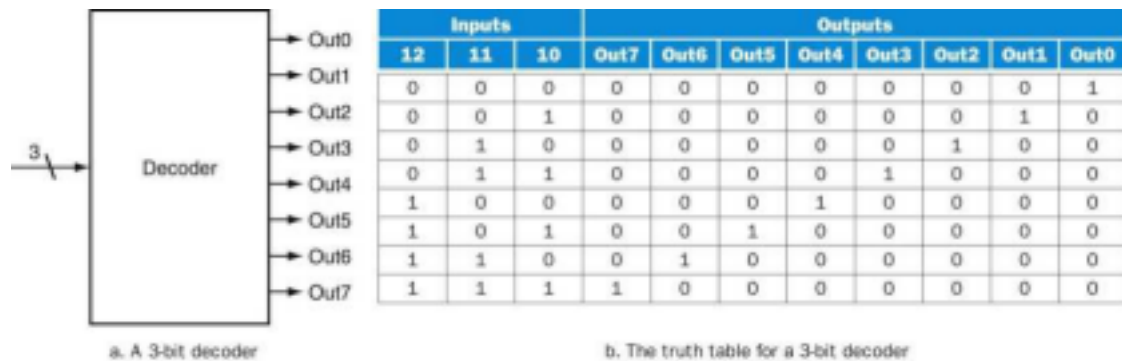


## decoder

A logic block that has an  $n$ -bit input and  $2n$  outputs, where only one output is asserted for each input combination.



**FIGURE A.3.1** A 3-bit decoder has three inputs, called 12, 11, and 10, and  $2^3 = 8$  outputs, called Out0 to Out7.

Only the output corresponding to the binary value of the input is true, as shown in the truth table. The label 3 on the input to the decoder says that the input signal is 3 bits wide.